

*Model Question Paper*  
**Microelectronics & VLSI Design**

*Time Allotted: 3 Hours*

*Full Marks : 70*

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

**GROUP – A**  
**(Multiple Choice Type Questions)**

1. Choose the correct alternatives for *any ten* of the following : 10×1=10
- i. Pseudo NMOS logic provides which of the following advantages?
    - a) Static power dissipation is less compared to CMOS logic
    - b) It is much faster compared to other logics
    - c) It requires less no. of transistors compared to CMOS logic
    - d) It is more noise immune.
  - ii. Which type of MOSFET exhibits no current at zero gate voltage?
    - a. Depletion MOSFET b. Enhancement MOSFET c. Both a and b d. None of the above
  - iii. For a symmetrical CMOS inverter the relation between aspect ratio of NMOS and PMOS is
    - a)  $(W/L)_P = (W/L)_N$     b)  $(W/L)_P = 2.5(W/L)_N$     c)  $2.5(W/L)_P = (W/L)_N$     d)  $(W/L)_P = 1/2.5(W/L)_N$
  - iv. Advantage of SRAM over DRAM is:
    - a) Very high speed.    b) Low cost per bit
    - c) Higher density    d) Less space required
  - v. Hierarchical decomposition of a large system in VLSI design is called
    - a) Modularity    b) Regularity    c) Locality    d) Decomposability
  - vi. What is the full form of FPGA ?
    - a) Field programmable gate array..
    - b) Full programmable gate array.
    - c) Fast programmable gate array .
  - vii. For a 2 inputs XOR gate what is the maximum nos. of MOS transistor.
    - a) 16    b) 8    c) 6    d) 10
  - viii. Which is not a part of FPGA?
    - a) Configurable logic block.

- b) IOB.
  - c) Microprocessor.
  - d) Routing Channels.
- viii. Which are the simple PLDS?
- a) CPLD. b)FPGA. c)CBIC. d)PLA.
- ix. How many CMOS Transistors are needed to implement XOR gates?
- a) 7 b)10 c)8 d)9
- x. What is ASIC?
- a) Application simplified IC. b) Applied IC. c) Application specific IC.
  - d) Authentic IC.
- xi. VLSI design flow is a
- a) cyclic process only b)parallel process c) sequential & cyclic process
  - d) none of these
- xii. VHDL is a
- a) Multi threaded program b) language like C c) single user program

**GROUP – B**

**(Short Answer Type Questions)**

Answer *any three* of the following.

3×5=15

2. Explain the operation of CMOS inverter with proper voltage transfer characteristic.
3. Explain how ON-resistance of a transmission gate changes as the input varies from 0 V to V<sub>dd</sub>, when the output has a light capacitive load.
4. Produce the XOR gate with 6 transistors CMOS TG.
5. Calculate the threshold voltage of a CMOS inverter.
6. Implement the following Boolean function with PLA
  - a)  $Y=ab + bc +ca$
  - b)  $F= ab' + abc'$


**GROUP – C**

**(Long Answer Type Questions)**

Answer any three of the following.

3×15=45

 7. a. Explain the n-well CMOS fabrication process with necessary diagram. 5  
 b.



Let  $V_{DD} = 5V$ ,  $V_{TH,1} = 1V$ ,  $k_{n,1}' = 20 \mu A/V^2$  and  $R = 1K \Omega$ .  
 What should be  $(W/L)_1$  needed for creating  $I_{ref} = 1mA$ ? 5

- c. Classify ASIC. Explain briefly the different ASIC. 5
8. a. Design AND, XOR gates using pass transistor logic. 5  
 b. design CMOS master slave D FF and describe its operation. 5  
 c. what do you mean by DCVSL design explain briefly with example. 5
9. a. Draw the VTC and explain different regions of CMOS inverter. Deduce the threshold voltage of CMOS inverter. 7+8
10. a. explain the pre-charge and evaluation for dynamic CMOS. 5  
 b. deduce the CMRR of CMOS differential amplifier. 10
11. a. explain the terms entity and architecture of VHDL program. 3  
 b. write a program to develop up counter using JK Flip flop using VHDL. 7  
 c. Explain the procedure of writing operation using SRAM.
12. Write short notes on the following:
- Explain is Channel-length modulation.
  - VHDL modeling of D-flip/flop.
  - Channel routing.
  - Layout of CMOS inverter.
  - Explain the FPGA architecture